

Department of Electronic and Telecommunication Engineering

University of Moratuwa, Sri Lanka

EN 2110 - Electronics - III



# Group Project

## Report

Submitted by

Thalagala B.P.

180631J

Submitted on

May 5, 2021

| Name           | Index   | Contribution |
|----------------|---------|--------------|
| Thalagala B.P. | 180631J |              |

Table 1: Contributions of each member

## Contents

|          |  |          |
|----------|--|----------|
| <b>1</b> | <b>Parasitic effect in Timing analysis</b> | <b>2</b> |
| 1.1      | System Design . . . . .                    | 2        |
| <b>2</b> | <b>PLD</b>                                 | <b>3</b> |
| 2.1      | Part 1 . . . . .                           | 3        |
| 2.2      | Part 2 . . . . .                           | 3        |
| 2.3      | Part 3 . . . . .                           | 3        |

# 1 Parasitic effect in Timing analysis

**Objective:** Design a 3 stage (3 inverters) ring oscillator. Find the correlation of the parasitic effect in the oscillation period.

## 1.1 System Design

Ring oscillator is a unstable, closed loop device with a negative feedback. It consists of an **odd number of identical inverters (NOT gates)** and its output oscillates between **two voltage levels** identified as high and low. The period of oscillation( $T$ ) of a ring oscillatoer can be expressed as follows where  $n$  is the number of cascaded NOT gates and  $\tau_{PD}$  is the propagation delay of a single inverter.

$$T = 2.n.\tau_{PD}$$

 


Figure 1: Waveform for Voltage of 3 stages CMOS Ring Oscillator

## 2 PLD

### 2.1 Part 1

**Objective:** *Design a programmable logic block to configure it as a ‘NAND’ or a ‘NOR’ gate using a single selection bit.*

### 2.2 Part 2

**Objective:** *Design a single switch matrix using six pass transistors.*

### 2.3 Part 3

**Objective:** *Design a PLD that can be used to design any 3 input combinational circuit.*