

Department of Electronic and Telecommunication Engineering

University of Moratuwa, Sri Lanka

EN 2110 - Electronics - III



Group Project

Report

Submitted by

Caldera H. D. J.	180079X
Oshan J. W. P.	180437U
Thalagala B.P.	180631J

Submitted on

May 6, 2021

Name	Index	Contribution
Caldera H. D. J.	180079X	
Oshan J. W. P.	180437U	
Thalagala B.P.	180631J	

Table 1: Contributions of each member

Contents

1	Parasitic effect in Timing analysis	2
1.1	System Design	2
1.2	simulation Results and Discussion	3
2	PLD	4
2.1	Part 1	4
2.2	Part 2	6
2.3	Part 3	11

1 Parasitic effect in Timing analysis

Objective: Design a 3 stage (3 inverters) ring oscillator. Find the correlation of the parasitic effect in the oscillation period.

1.1 System Design

Ring oscillator is a unstable, closed loop device with a negative feedback. It consists of an **odd number of identical inverters (NOT gates)** and its output oscillates between **two voltage levels** identified as high and low. The period of oscillation(T) of a ring oscillatoer can be expressed as follows where n is the number of cascaded NOT gates and τ_{PD} is the propagation delay of a single inverter.

$$T = 2.n.\tau_{PD}$$

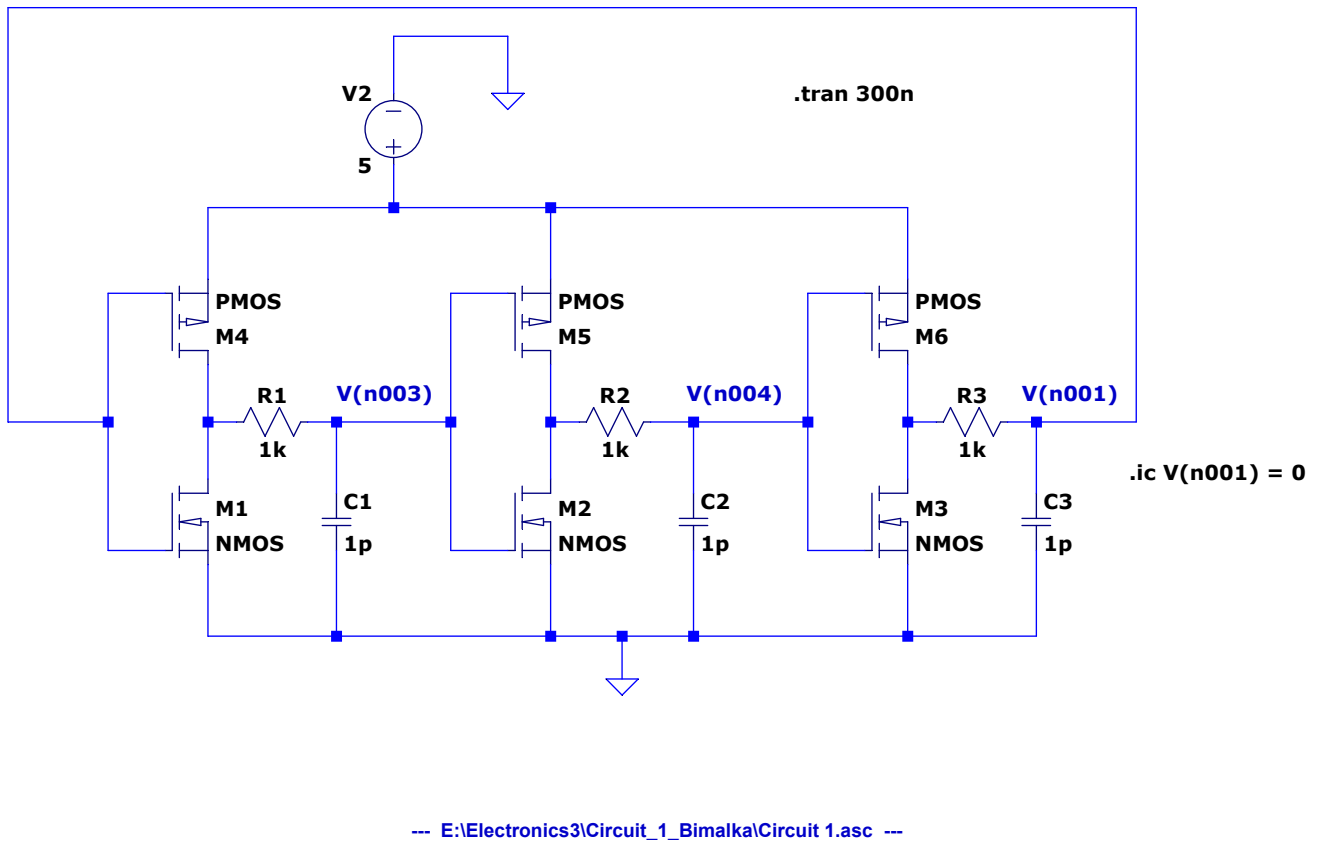


Figure 1: 3 stages enhanced CMOS Ring Oscillator

1.2 simulation Results and Discussion

 


Figure 2: Waveform for Voltages of 3 stages enhanced CMOS Ring Oscillator

2 PLD

2.1 Part 1

Objective: Design a programmable logic block to configure it as a 'NAND' or a 'NOR' gate using a single selection bit.

First a truth table is drawn for this part considering a single selection bit (S) with two inputs (A, B) such that S=0 for 'NAND' and S=1 for 'NOR' operations respectively.

S	A	B	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

Table 2: The truth table

Then the relevant logic expression was obtained using a karnaugh map and it was further simplified to obtain the combination of 'NAND' and 'NOR' operations.


S\AB	00	01	11	10
0	1	1	0	1
1	1	0	0	0

Table 3: Karnaugh Map for the above truth table


$$\begin{aligned}
 F &= \overline{S}.\overline{A} + \overline{S}.\overline{B} + \overline{A}.\overline{B} \\
 &= \overline{S}.(\overline{A} + \overline{B}) + \overline{A}.\overline{B} \\
 &= \overline{S}.(\overline{A.B}) + \overline{A} + \overline{B} \\
 &= \overline{S + A.B} + \overline{A} + \overline{B} \\
 &= \overline{(S + A.B).(A + B)} \\
 &= \overline{(S + \overline{A.B}).(\overline{A} + \overline{B})}
 \end{aligned}$$

So, the resultant combinational logic circuit is as follows. (2 NANDs, 2 NORs, 3 NOTs)

 
For the implementation of this circuit; 'NOT', 'NAND', and 'NOR' gates were designed using 'NMOS' and 'PMOS' transistors. Their schematics in LTspice are depicted below.



(a) Schematic of NOT gate

 

(b) Schematic of NAND gate

 

(c) Schematic of NOR gate

Figure 3: Basic Gates in the CMOS logic

Finally, the PLD block is designed using the above gates and the waveforms were obtained.

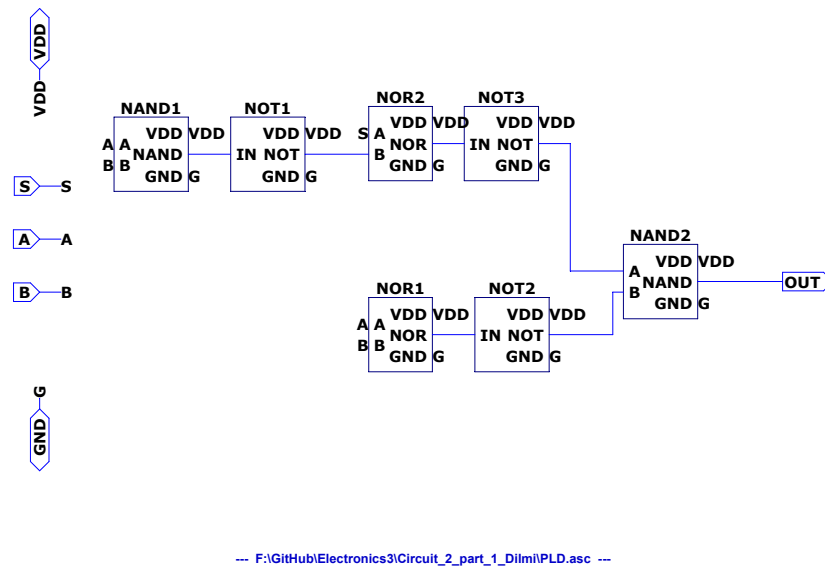


Figure 4: Circuit designed using logic blocks

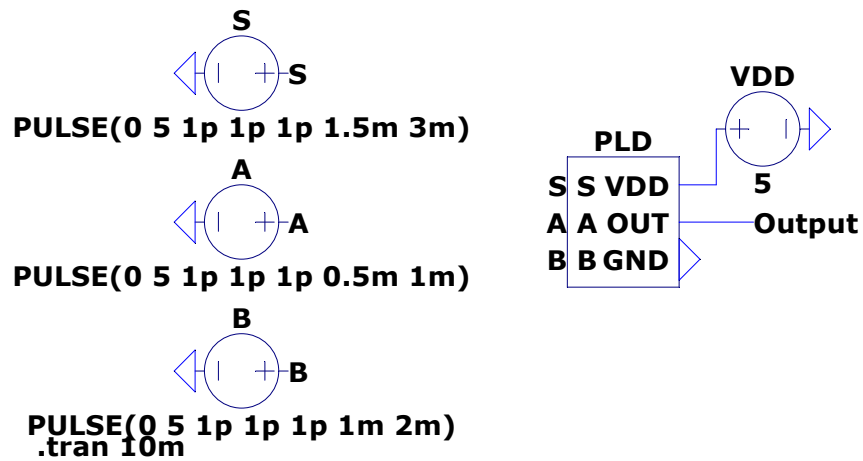


Figure 5: Designed PLD block


 


Figure 6: Waveforms for inputs and output of PLD

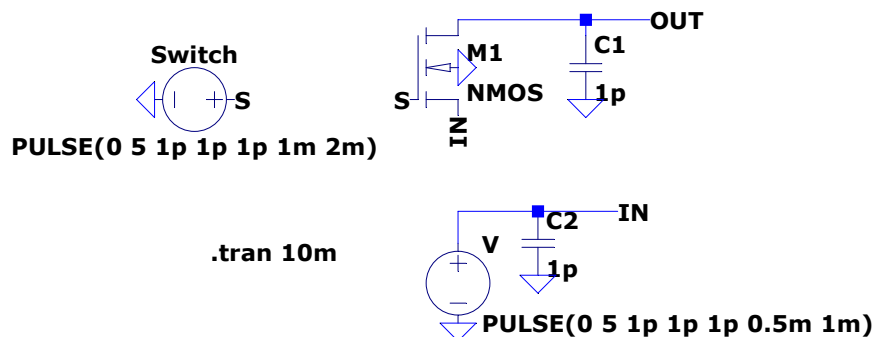2.2 Part 2

Objective: *Design a single switch matrix using six pass transistors.*

In this part, the single switch matrix is needed to be designed using six pass transistors. So as the first step, a pass transistor was designed and its performance was checked. Simply an 'NMOS' transistor is fed with a switch, could be used for this task. So when the switch is on, the input signal will be received at the output (Threshold voltage is considering as zero since an ideal nmos). Also capacitors were used to ground the high impedance state which occurred when the NMOS is OFF.



--- F:\GitHub\Electronics3\Circuit_2_part_2_Dilmi\pass_ttr.asc ---

Figure 7: Schematic diagram of the pass transistor

 


Figure 8: Waveform of the pass transistor

Then using six such transistors, the single switch matrix was designed and the schematic diagram of it is shown below.

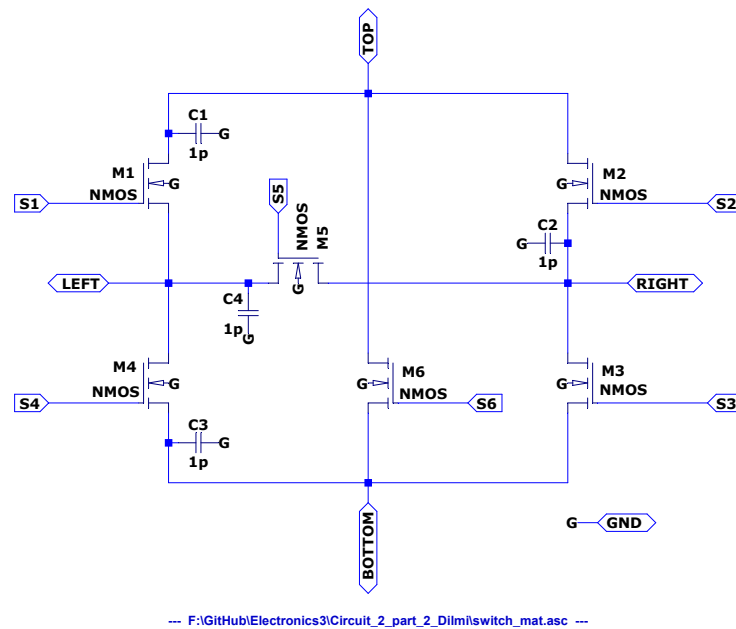


Figure 9: Schematic diagram of the single switch matrix

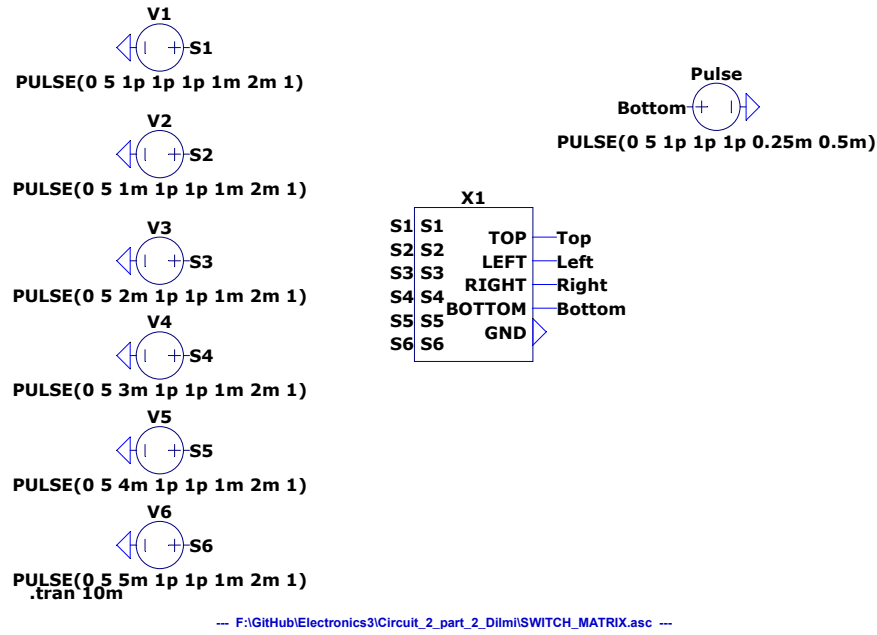


Figure 10: Designed single switch matrix block

Finally the functionality of the circuit was checked by giving pulses to left, right, top, and bottom corners separately and switching on the switches at different periods.

 


Figure 11: Waveforms when the top terminal is fed with a pulse

 


Figure 12: Waveforms when the left terminal is fed with a pulse

 


Figure 13: Waveforms when the right terminal is fed with a pulse

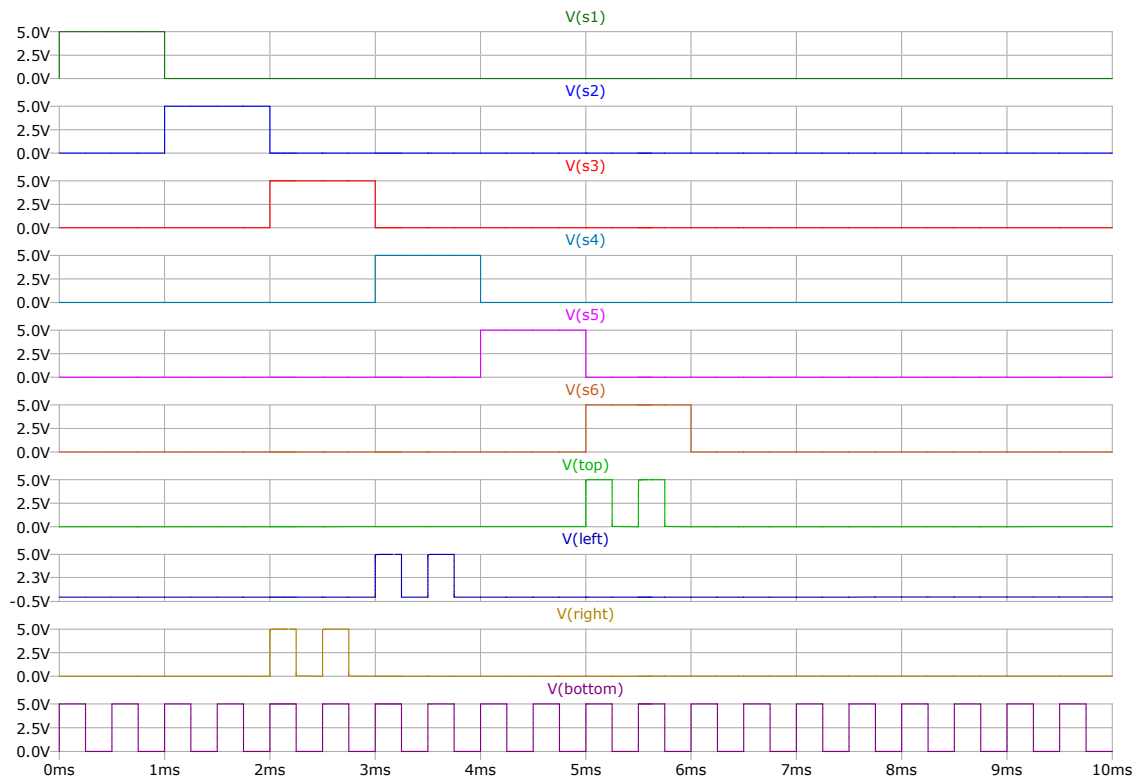


Figure 14: Waveforms when the bottom terminal is fed with a pulse

2.3 Part 3

Objective: *Design a PLD that can be used to design any 3 input combinational circuit.*

The task was to design a PLD circuit capable of implementing any three input combinational circuit. The truth-table of any three input combinational circuits will be as below.

A	B	C	Output
0	0	0	S_1
0	0	1	S_2
0	1	0	S_3
0	1	1	S_4
1	0	0	S_5
1	0	1	S_6
1	1	0	S_7
1	1	1	S_8

Table 4: The truth-table of any three input combinational circuit


Outputs S_1, S_2, \dots, S_8 differ with the combinational circuit. So we can write an expression for the combinational logic circuit using the 8 minterms. Which minterms to be selected differ according to the S_1, S_2, \dots, S_8 . If any S_i is 1 then the corresponding minterm is taken into the sum of products expression. If S_i is 0 that corresponding minterm is discarded.

So we can build the PLD with a fixed AND plane which has all eight minterms and a programmable OR plane which can be programmed using S_i terms. So our PLD becomes a PROM.

Before building the PLD the AND plane and OR plane should be created. For the fixed AND plane, we need eight minterms. A minterm is a product of any three of $A, \bar{A}, B, \bar{B}, C$ or \bar{C} . So we need three input and gate. We configured a three-input AND gate using NAND, NOR, and NOT gates as below for better efficiency.

$$A.B.C = \overline{\overline{A.B.C}} = \overline{\overline{A.B} + \overline{C}}$$

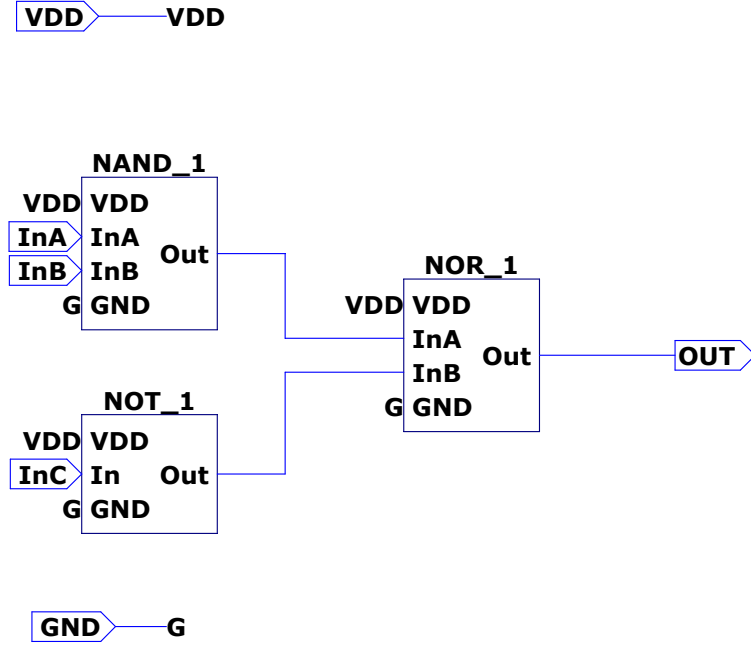Using this expression we constructed the 3 input AND gates using a minimum number of logic gates.




--- D:\acalgithub\electronics3\circuit_2_part_3_oshan3_and.asc ---

Figure 15: Implementing the three-input AND gate using NOR, AND, and NOT gates.

Using seven separate OR gates(7 NOR gates + 7 NOT gates) to implement the OR plane, increases complexity and the latency of the circuit by a huge factor. Instead, we can simplify the expression and use a minimum number of gates as below.

$$\begin{aligned}
 &= S_1 + S_2 + S_3 + S_4 + S_5 + S_6 + S_7 + S_8 \\
 &= \overline{\overline{S_1 + S_2 + S_3 + S_4 + S_5 + S_6 + S_7 + S_8}} \\
 &= \overline{(S_1 + S_2 + S_3 + S_4) \cdot (S_5 + S_6 + S_7 + S_8)} \\
 &= \overline{(S_1 + S_2) \cdot (S_3 + S_4) \cdot (S_5 + S_6) \cdot (S_7 + S_8)} \\
 &= \overline{(S_1 + S_2) \cdot (S_3 + S_4)} + \overline{(S_5 + S_6) \cdot (S_7 + S_8)} \\
 &= \overline{\overline{(S_1 + S_2) \cdot (S_3 + S_4)}} + \overline{\overline{(S_5 + S_6) \cdot (S_7 + S_8)}}
 \end{aligned}$$

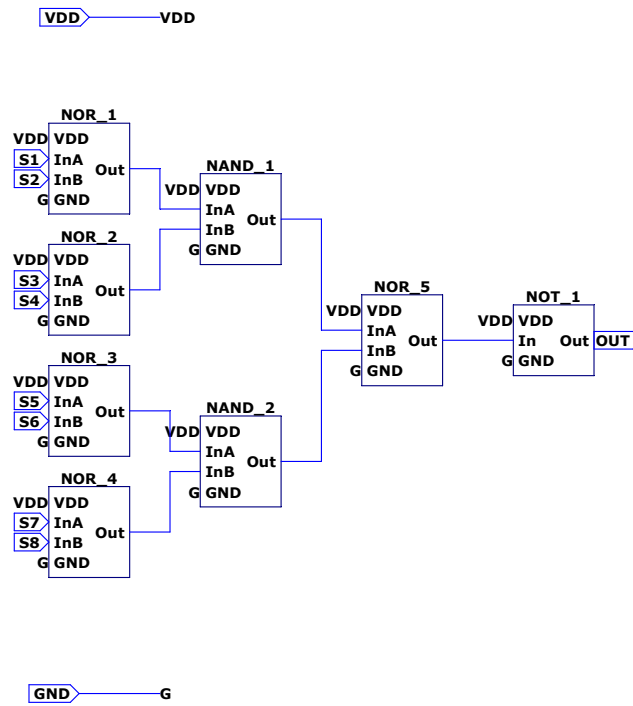Using this expression we were able to build an OR plane with a minimum number of components as below.




--- D:\aca\github\electronics3\circuit_2_part_3_oshan\8_or.asc ---

Figure 16: Implementing the OR plane

Instead of using a total of 14 logic gates, now we have implemented it using only 8 logic gates. This reduces the latency and complexity by a huge factor.

PROM is constructed as below

 

--- D:\aca\github\electronics3\circuit_2_part_3_oshan\prom.asc ---

Figure 17: PROM circuit

We have used nmos transistors as switches which choose, which minterms are taken into the sum of products. We didn't choose passgates as switches as it increases the complexity and the latency of the circuit.

We tested the circuit for different combinational circuits by configuring Si switches. Below we have configured the PROM as a simple NOR gate.

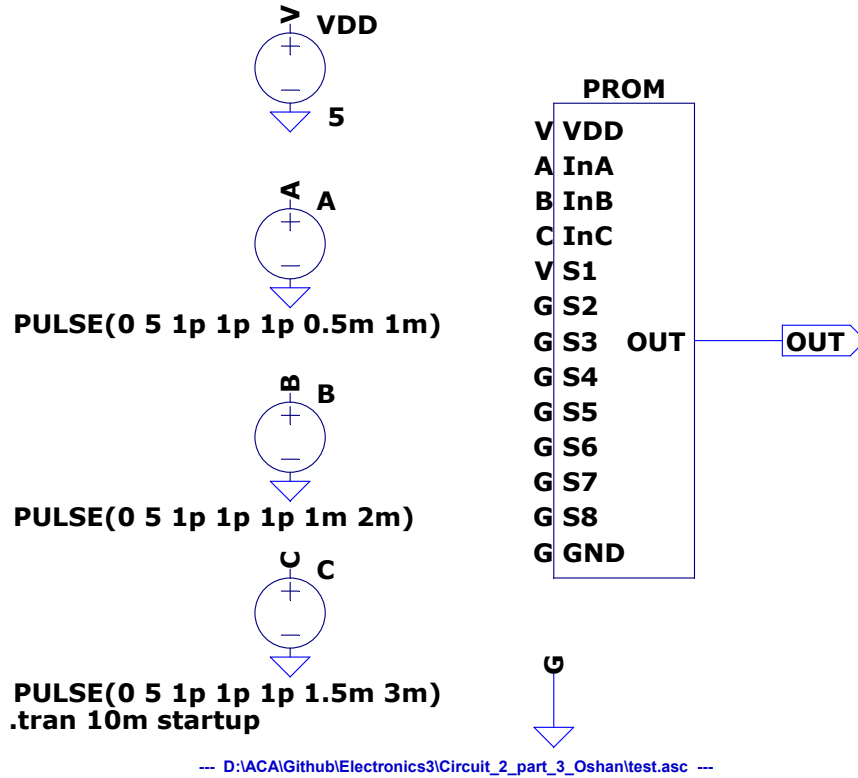


Figure 18: PROM configured as a NOR gate

Results were as below,

 


Figure 19: Results of PROM configured as a NOR gate

We can observe that the PROM is functioning correctly.